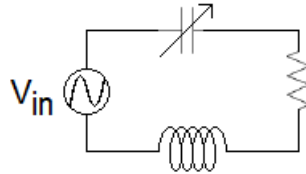


Electronics

AC circuits

Problem 1.- An RLC circuit consists of the devices shown in the figure, with values $R = 10\text{k}\Omega$, $L = 15\text{mH}$, and C a variable capacitance. The AC voltage source supplies a signal with amplitude of 2 volts and angular frequency 1,500 radians per second. For what value of C is the amplitude of the current maximum?



Solution: The maximum current corresponds to the resonance point, which will happen when the capacitor and inductor impedances are equal in magnitude:

$$\frac{1}{\omega C} = \omega L \rightarrow C = \frac{1}{\omega^2 L} = \frac{1}{(1,500\text{rad / s})^2 (15 \times 10^{-3}\text{H})} = \mathbf{30\ \mu\text{F}}$$

Problem 2.- A fixed capacitance of 66nF is used together with a variable inductor in the tuning section of a radio. What inductance tunes the circuit into the signal from a radio station broadcasting at 575 kHz?

Solution: Angular frequency: $\omega = 2\pi f = 2(3.1416)(575 \times 10^3\text{Hz}) = 3.61 \times 10^6\text{rad / s}$

$$\text{Since } \omega = \frac{1}{\sqrt{CL}} \rightarrow L = \frac{1}{\omega^2 C} = \frac{1}{(3.61 \times 10^6\text{rad / s})^2 (0.066 \times 10^{-6}\text{F})} = \mathbf{1.16\ \mu\text{H}}$$