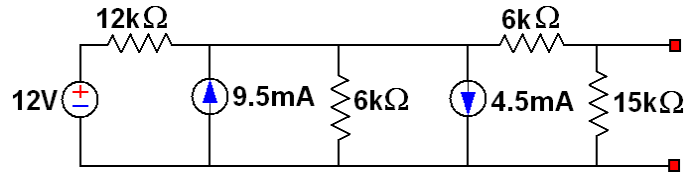



Electronics

Thevenin equivalent

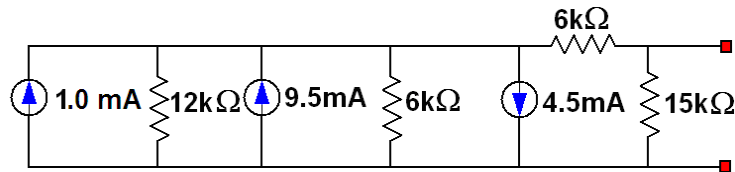Problem 1.- Find the simplest equivalent of the following circuit from the point of view of the terminals on the right side:



Solution: To simplify the circuit, let us convert the voltage source to a current source, giving the equivalent:




Now we can combine all the current sources that are in parallel and all the resistors in parallel on the left side of the circuit to give:


$$I = 1.0\text{mA} + 9.5\text{mA} - 4.5\text{mA} = 6.0\text{mA}$$

$$R = \frac{1}{\frac{1}{12\text{k}\Omega} + \frac{1}{6\text{k}\Omega}} = 4\text{k}\Omega$$

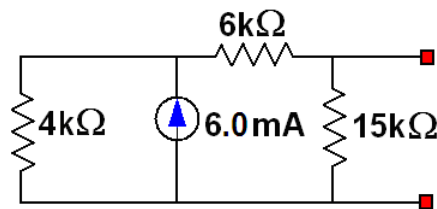With these changes, the circuit looks like this:



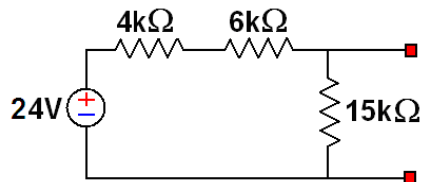We can go back to a voltage source, replacing the 4k-ohm resistor in parallel with the 6mA source by a 24V source in series with a 4k-ohm resistor:




We use the rule of voltage divider to calculate the Thevenin voltage:


$$V_{Thevenin} = 24V \left(\frac{15k\Omega}{15k\Omega + 6k\Omega + 4k\Omega} \right) = 14.4V$$

The Thevenin resistance is obtained after replacing the voltage source by a short circuit and calculating the resistance from the point of view of the terminals:


$$R_{Thevenin} = \frac{1}{\frac{1}{15k\Omega} + \frac{1}{10k\Omega}} = 6k\Omega$$

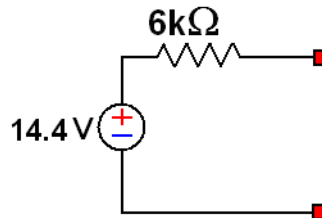

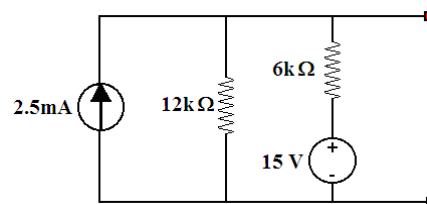Problem 2.- Find the Thevenin equivalent of the following circuit:



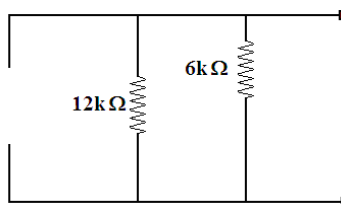
Solution: First, let us find the Thevenin resistance. We open the current sources and short the voltage sources



Obtaining

$$R_{Thevenin} = \frac{1}{\frac{1}{12k\Omega} + \frac{1}{6k\Omega}} = 4k\Omega$$

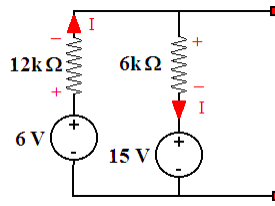To get the Thevenin voltage we convert the current source in parallel with the 12kΩ resistor to a voltage source with a value of $2.5mA \times 12k\Omega = 6V$ in series with the same resistor:




A loop equation for this circuit gives us:

$$6V - 12k\Omega I - 6k\Omega I - 15V = 0 \rightarrow I = -9V / 18k\Omega = -0.5mA$$


This allows us to calculate the Thevenin voltage:

$$V_{Thevenin} = 15V + 6k\Omega I = 15V + 6k\Omega(-0.5mA) = 12V$$

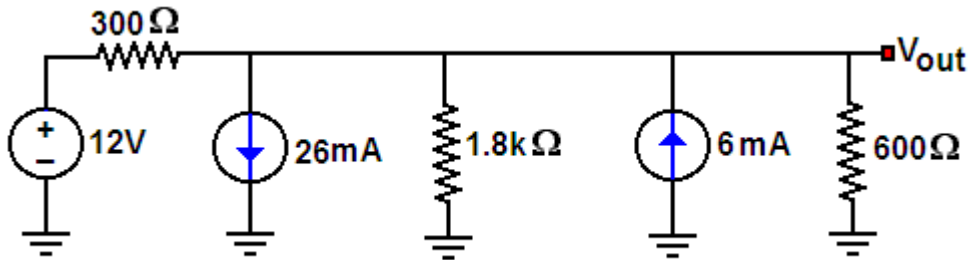Problem 3.- Find the Thevenin equivalent of the following circuit:



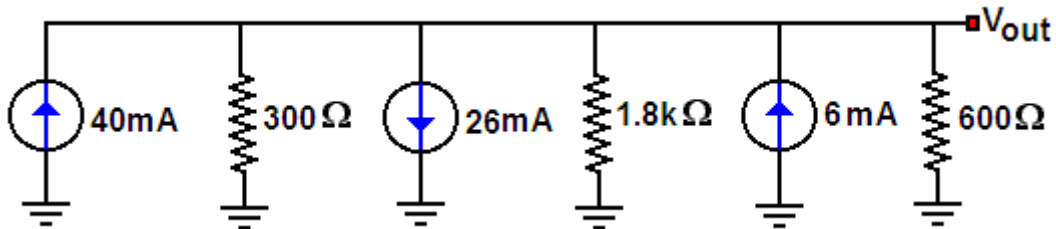Solution: We convert the voltage source to a current source, so the circuit becomes the following:



Recall that in this conversion, the resistance stays the same and the voltage source in series is replaced by a current source in parallel with a value of V/R .


The advantage of this change is that now there are three resistors in parallel whose equivalent value is:

$$R_{equivalent} = \frac{1}{\frac{1}{300\Omega} + \frac{1}{1800\Omega} + \frac{1}{600\Omega}} = 180\Omega$$


The current sources are also in parallel, so their equivalent is just one current source with the sum of their currents (considering their orientation).

$$I_{\text{equivalent}} = 40\text{mA} - 26\text{mA} + 6\text{mA} = 20\text{mA}$$


So the equivalent circuit becomes:

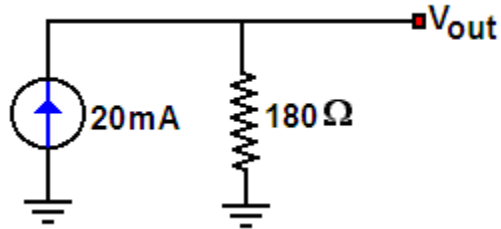


This circuit can also be converted to a Thevenin equivalent by keeping the same resistance and replacing the current source by a voltage source of value RI , as follows:

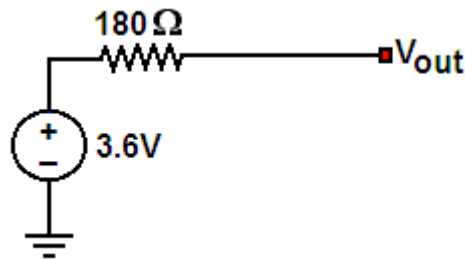

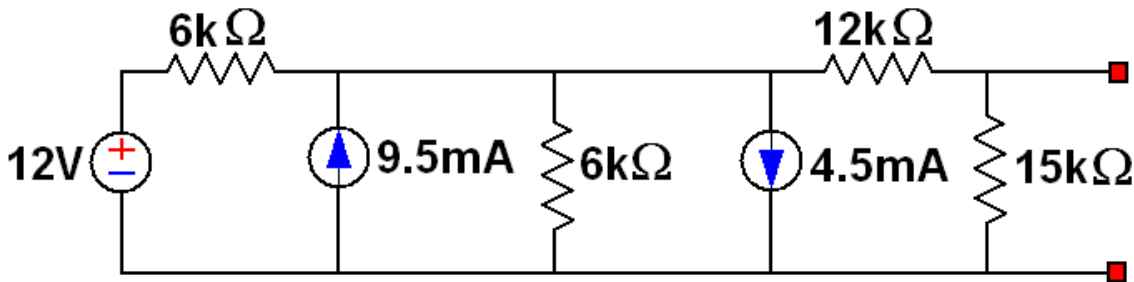Problem 4.- Find the simplest equivalent of the following circuit:



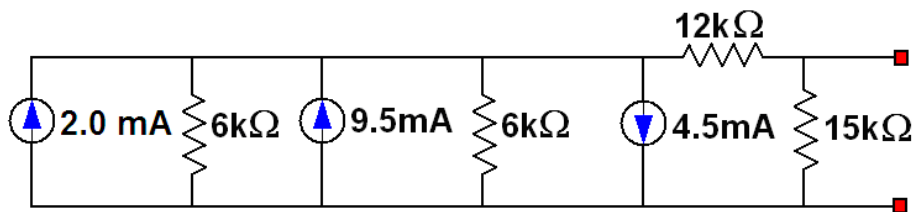Solution: Similar to what was done above, let us convert the voltage source to a current source, giving the equivalent:




Now we can combine all the current sources and all the resistors in parallel to give:


$$I = 2.0\text{mA} + 9.5\text{mA} - 4.5\text{mA} = 7.0\text{mA}$$

$$R = \frac{1}{\frac{1}{6\text{k}\Omega} + \frac{1}{6\text{k}\Omega}} = 3\text{k}\Omega$$

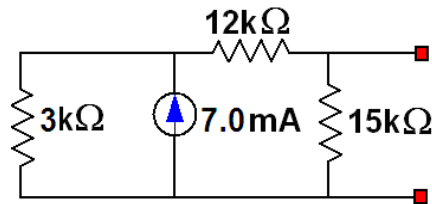With these changes, the circuit looks like this:



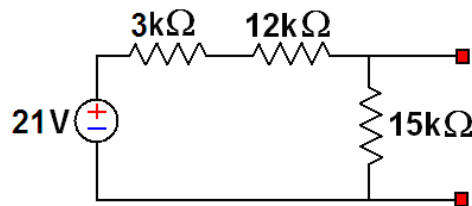We go back to a voltage source, replacing the 3k-ohm resistor in parallel with the 7mA source by a 21V source in series with a 3kohm resistor, to get:



The Thevenin voltage is calculated using the rule of a voltage divider:

$$V_{Thevenin} = 21V \left(\frac{15\text{k}\Omega}{15\text{k}\Omega + 12\text{k}\Omega + 3\text{k}\Omega} \right) = 10.5V$$

And the Thevenin resistance is obtained after replacing the voltage source by a short circuit:

$$R_{Thevenin} = \frac{1}{\frac{1}{15\text{k}\Omega} + \frac{1}{15\text{k}\Omega}} = 7.5\text{k}\Omega$$

Giving the final equivalent circuit:

