

Electronics


Common collector amplifier

Problem 1.- An *emitter follower* is an amplifier that has a typical voltage gain of less than 1 that you can build with one transistor. Why would you want such a thing?


Solution: When you want to couple a high output impedance signal to a low impedance load the *emitter follower* gives you the solution.

Problem 2.- Assume the capacitors in the following circuit behave as short circuits at the signal frequency. Find

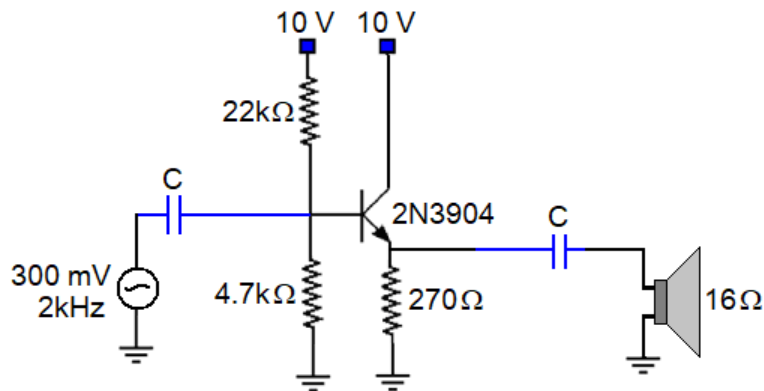- (a) The voltage gain of the amplifier
- (b) The input impedance of the circuit and
- (c) The gain in power obtained this way.



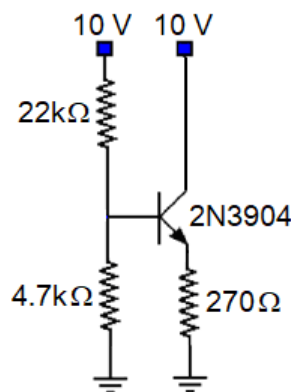
Solution: First we carry out the **DC analysis**. The capacitors behave like open circuits and so the equivalent circuit looks like this:



The base side of the transistor can be replaced by a Thevenin equivalent, where:

$$R_{Thevenin} = \frac{1}{\frac{1}{22k\Omega} + \frac{1}{4.7k\Omega}} = 3.87k\Omega \quad \text{and} \quad V_{Thevenin} = 10V \left(\frac{4.7k\Omega}{22k\Omega + 4.7k\Omega} \right) = 1.76V$$

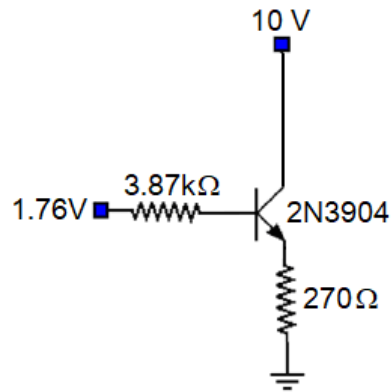With these changes the equivalent circuit will be:



The equation for the voltage on the base side is:

$$1.76V = 3.87k\Omega I_B + 0.7V + 270\Omega I_E$$

But $I_E \approx \beta I_B$, so:

$$1.76V = 3.87k\Omega I_B + 0.7V + 270\Omega \beta I_B$$

$$I_B = \frac{1.76V - 0.7V}{3.87k\Omega + 270\Omega \beta}$$

We need the value of the current gain to find the base current. If we assume $\beta = 200$, which is the typical value according to the specs of this transistor, we get:


$$I_B = \frac{1.76V - 0.7V}{3.87k\Omega + 200 \times 270\Omega} = 18.3\mu A$$

The voltage collector emitter can be calculated now:

$$V_{CE} = 10V - 270\Omega I_E = 10V - 270\Omega (200 \times 18.3\mu A) = 9.0V$$

This is not the best operating point, but it is still in the active region.

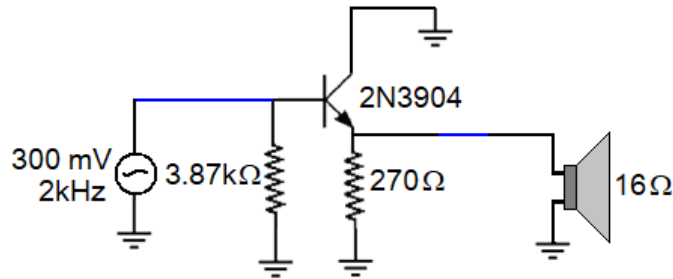
Now, the **AC analysis**. Recall that the capacitors behave like short-circuits and all voltage DC sources are replaced by short circuits:



The transistor is replaced by a model where the base-emitter junction is a resistor of value


$$r_d = \frac{25mV}{I_B} = \frac{25mV}{18.3\mu A} = 1.36k\Omega \text{ and the collector-emitter is a current source of value}$$

$$i_C = \beta i_B = 200i_B :$$

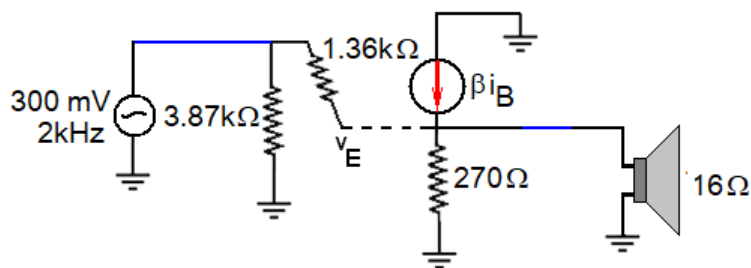

Notice that the load (the speaker) is in parallel with the 270-ohm resistor, so they give an equivalent of:
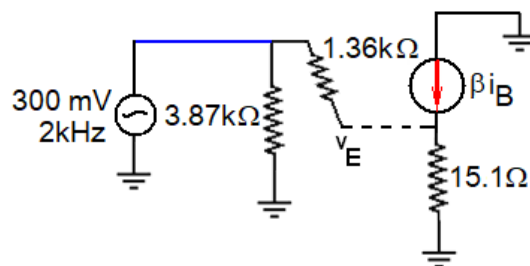
$$R_{Equivalent} = \frac{1}{\frac{1}{270\Omega} + \frac{1}{16\Omega}} = 15.1\Omega, \text{ so the simplified circuit looks as follows:}$$



To calculate the voltage gain, notice that we can write an equation for the loop source-base-emitter-ground:

$$300mV = 1.36k\Omega i_B + 15.1\Omega i_E = 300mV = 1.36k\Omega i_B + 15.1\Omega(200i_B)$$

$$\rightarrow i_B = \frac{300mV}{1.36k\Omega + 200 \times 15.1\Omega} = 68.5\mu A$$

$$\text{So the load voltage is: } V_L = 15.1\Omega i_E = 15.1\Omega(200 \times 68.5\mu A) = 207mV$$

$$\text{As expected the gain in voltage is less than one: } A = \frac{207mV}{300mV} = \mathbf{0.69}$$

To calculate the input impedance, notice that the 15.1 ohm resistor behaves like a resistor of value $r = \beta \times 15.1\Omega = 200 \times 15.1\Omega = 3,020\Omega$ from the point of view of the base. This resistor is in series with the 1.36kohm resistor, giving a value of 4.38kohm. And the combination is in parallel with the 3.87kohm resistor giving an input impedance of:

$$R = \frac{1}{\frac{1}{4.38k\Omega} + \frac{1}{3.87k\Omega}} = 2.05k\Omega$$

The load impedance is still 16 ohms and the gain in power is:

$$A_{power} = \frac{P_{load}}{P_{source}} = \frac{\frac{(207mV)^2}{16\Omega}}{\frac{(300mV)^2}{2.05k\Omega}} = \mathbf{61.1}$$