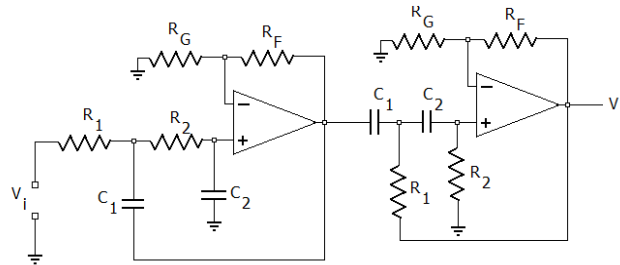


# Electronics

## Band pass filter

**Problem 1.-** For a PLC (Power Line Carrier) application, design a band pass filter from 200kHz to 300kHz and drops of 40dB per decade on both sides of the band. Use only two opamps.

**Solution:** The solution uses two active filters with two poles, as shown below:



The first stage is the low pass filter and we select the components to have a cutoff frequency of 300kHz

$$R_1 C_1 = R_2 C_2 = \frac{1}{2\pi \times 300 \text{kHz}}$$

For example with  $R = 3.3\text{k}\Omega$  and  $C = 160\text{pF}$


For the second stage  $R = 3.6\text{k}\Omega$  and  $C = 220\text{pF}$  will give 200kHz of cutoff frequency.

$R_G$  and  $R_F$  can give an additional gain in the middle of the band, but that is not required in this application.

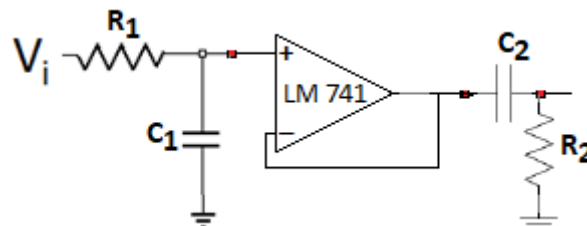**Problem 2.-** A selective voltmeter should read the voltage in a range of frequencies from 200kHz to 240kHz.

- Design a band pass filter with those two cutoff frequencies and drop of 20dB per decade on each side of the band.
- Calculate the gain in the middle of the band at 220kHz.

**Solution:** A simple low pass RC filter connected through a voltage follower with another RC filter can do what we need. The low pass filter is set to 240kHz and the high pass to 200kHz.



For example using these values

$$R_1 = 660\Omega$$

$$R_2 = 790\Omega$$

$$C_1 = 1nF$$


$$C_2 = 1nF$$

The gain at 220kHz is

$$\frac{v_o}{v_i} = \frac{1}{\sqrt{1 + \left(\frac{220kHz}{240kHz}\right)^2}} \cdot \frac{1}{\sqrt{1 + \left(\frac{200kHz}{220kHz}\right)^2}} = 0.545$$

This is a drop of 5 dB.

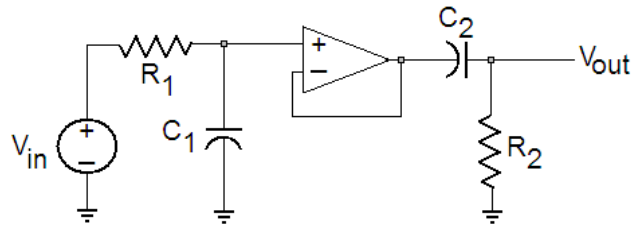**Problem 3.-** In the following band-pass filter you want the low cut-off frequency to be 2kHz and the upper cut-off to be 15kHz.



(a) Find reasonable values of  $R_1$ ,  $C_1$ ,  $R_2$  and  $C_2$  to get the desired response.

(b) What is the gain for a frequency of 20 kHz?

**Solution:**

The combination  $R_1$  and  $C_1$  behaves as a low pass filter, so we want:


$$15kHz = \frac{1}{2\pi R_1 C_1} \rightarrow R_1 = \frac{1}{2\pi C_1 (15kHz)}, \text{ for example } 22nF \text{ and } 480\Omega$$

The combination  $R_2$  and  $C_2$  behaves as a high pass filter, and here we want:

$$2kHz = \frac{1}{2\pi R_2 C_2} \rightarrow R_2 = \frac{1}{2\pi C_2 (2kHz)}, \text{ for example } 22nF \text{ and } 3.6k\Omega$$

The gain for a frequency of 20 kHz is 0.6 or -4.4dB

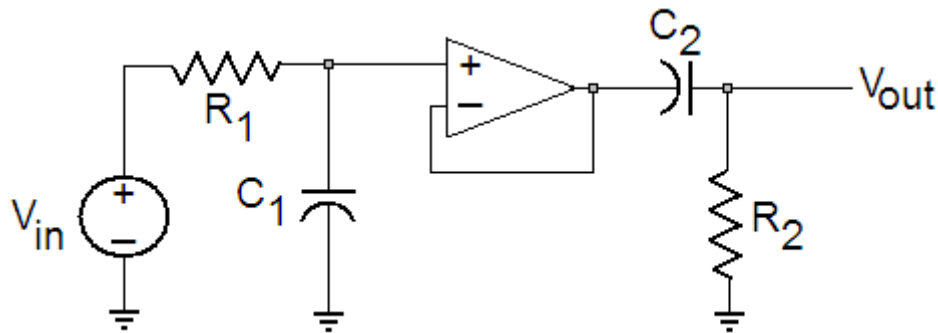**Problem 4.-** In the following band-pass filter the values of the resistors and capacitors are as follows:  $C_1 = 22\text{nF}$   $R_1 = 330\Omega$   $C_2 = 470\text{nF}$   $R_2 = 1.0\text{k}\Omega$



- Find the high and low cut-off frequencies.
- Graph the gain as a function of frequency.
- What is the gain for a frequency of 300Hz?

**Solution:** The circuit on the left of the opamp will behave as a low pass filter with a cutoff frequency of:

$$f_2 = \frac{1}{2\pi R_1 C_1} = \frac{1}{2\pi(330\Omega)(22\text{nF})} = 21,900 \text{ Hz}$$


On the other hand, the circuit on the right of the opamp will behave as a high pass filter with a cutoff frequency of:

$$f_1 = \frac{1}{2\pi R_2 C_2} = \frac{1}{2\pi(1\text{k}\Omega)(470\text{nF})} = 340 \text{ Hz}$$


The overall gain will be:

$$A = \left[ \frac{1}{\sqrt{1 + (f / 21,900)^2}} \right] \left[ \frac{1}{\sqrt{1 + (340 / f)^2}} \right]$$

Whose graph looks as follows:

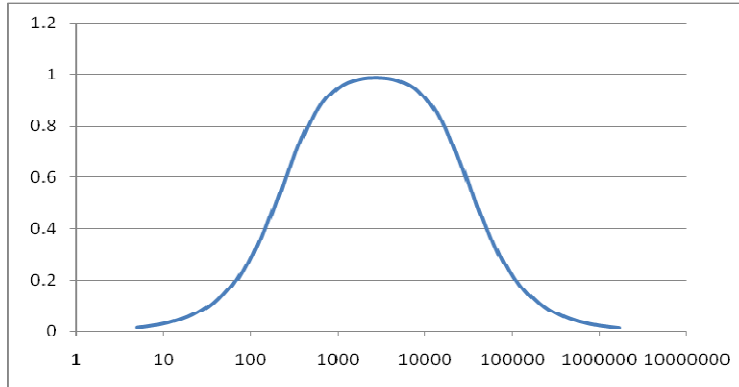

In decibels the graph will be:

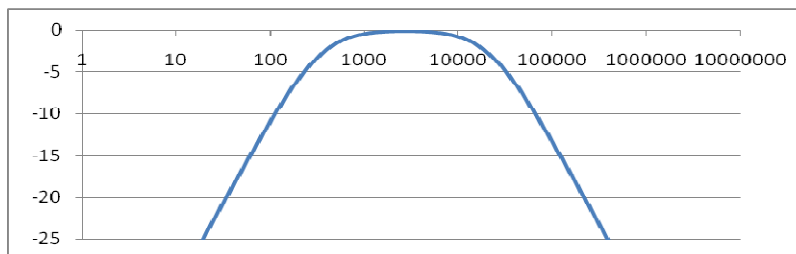

**At 300 Hz the gain is 0.66 or -3.6dB**