

Electronics

High pass filters

Problem 1.- Design a high pass filter with the Bode diagram given below.

