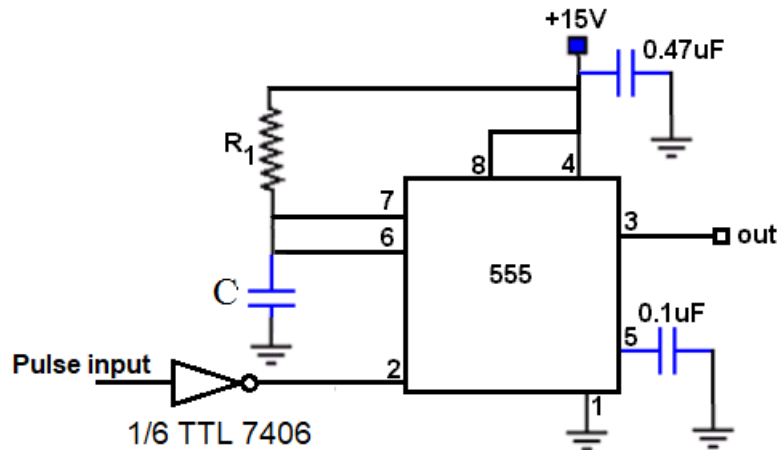


Electronics

One shot with a 555 chip

Problem 1.- In an application for a soda expending machine you need that a valve to open for 2.25s each time a *positive* pulse is received. Design a circuit that takes the input signal and produces a TTL output that will control the relay for the valve.

Solution: One solution is to use the 555 chip in the mono-stable configuration (one-shot) but after inverting the pulse to make it a negative one. We select the capacitor and resistance to obtain the 2.25 seconds.



The values should be such that


$$2.25s = \ln(3)R_1C$$

For example 47µF and 43kohm.

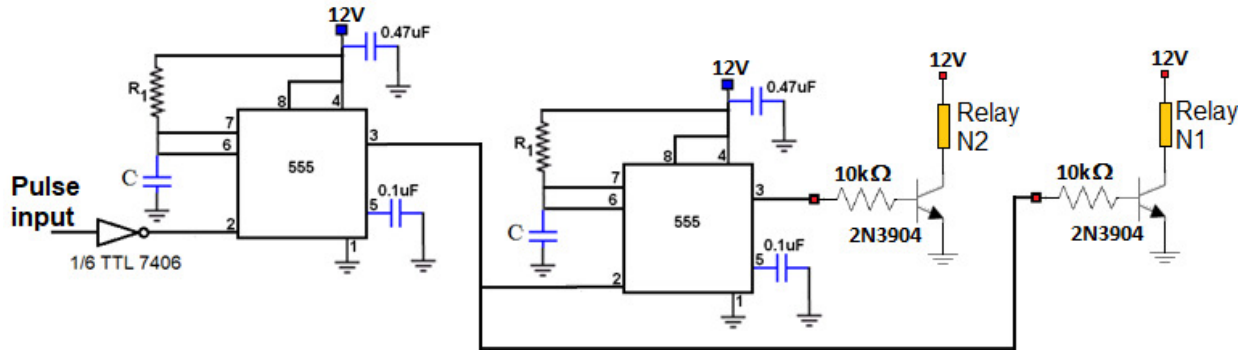Problem 2.- Consider the following application for a potato chips bagging device: When pressing a button, relay N1 (filling) has to be on for 1s and after it turns off, relay N2 (sealing) also turn on for 1s.

Design a circuit that follows that sequence. The relays require 40mA at 12V.

Solution: There are multiple possible solutions to this problem. Here is one idea: Two “one-shot” circuits of 1 second each, where the first one triggers the second.



To obtain the required time we need:

$$T = \ln(3)R_1C \rightarrow R_1C = 0.91s$$

This could be done with $100\mu\text{F}$ and $9.1\text{k}\Omega$.


Notice that the relays take their current from the collector of 2N3904 transistors, which are taken to saturation by the 555 chips outputs.

Problem 3.- Design a circuit that triggers a 10ms output when receiving a short input pulse

Problem 4.- In a coffee expending machine it is required that when pressing a button, a valve is open for 10 seconds (to let coffee fill a cup) and another valve for two seconds (to add the cream). Design a circuit with this behavior. The output can be relays or open collectors that can handle 40mA.

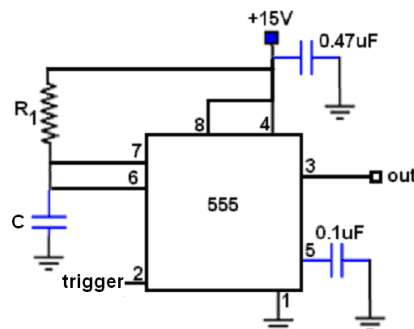Problem 5.- In a safety device in a re-tiring factory, a motor needs to be reversed in an emergency when a security bar is pressed. To do this you need to design a circuit that, when a pulse is received the output should be on for three seconds regardless of the width of the input pulse.

Solution: The solution can be done using the chip 555 in a one-shot configuration as shown below:



After a pulse is received at pin 2, the output turns on during a time given by:

$$t_{width} = R_1C \ln(3) = 1.1R_1C$$

If we need a pulse width of 3s we can select $C=4.7\mu\text{F}$ and

$$R_1 = \frac{t_{width}}{C \ln(3)} = \frac{3s}{1.1(4.7 \times 10^{-6} F)} = 580\text{k}\Omega$$

A commercial value close to this is $560\text{k}\Omega$.

Problem 5a.- Design a one-shot circuit with a width of 50ms. Sketch the circuit and select the values of the components.

Solution: The following circuit behaves as a one-shot with a width of

$$t_{width} = R_1 C \ln(3) = 1.1 R_1 C$$

If we want 50ms we can select $C = 1\mu\text{F}$ and $R_1 = \frac{t_{width}}{C \ln(3)} = \frac{50 \times 10^{-3} s}{1.1(1 \times 10^{-6} F)} = 45\text{k}\Omega$

