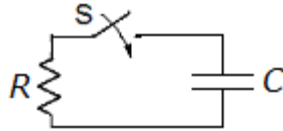


# Physics II

## RC Circuits

These electric circuits contain a combination of resistors and capacitors. Consider the following circuit.



Let's say the capacitor initially has a charge  $q$  and hence an initial voltage  $V_o = \frac{q}{C}$ , but at time  $t=0$  the switch  $S$  is closed.

Initially, the current will be  $i = \frac{V_o}{R}$ , but this current will discharge the capacitor, which in turn will reduce the voltage reducing the current as well.

While the capacitor is discharging, the circuit equation will be:

$$\frac{dV}{dt} = -\frac{V}{RC}$$

The minus sign is because the current is due to the capacitor discharge  $i = -dq/dt$  and the charge in the capacitor is  $q = CV$ .

This is an ordinary first order differential equation, whose solution is an exponential function:

$$V = V_o \exp(-t/\tau)$$


Where  $\tau = RC$  is the time constant of the circuit. Notice that 1 farad times 1 ohm is 1 second.

Similarly, the current will decrease exponentially:

$$i = \frac{V_o}{R} \exp(-t/\tau)$$

If the initial conditions or final conditions are different, the solution is similar with the same time constant.

For example, let's examine this circuit:

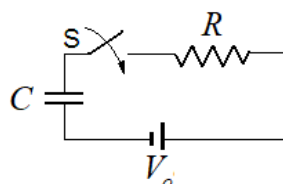

In this case the capacitor is initially discharged and at  $t=0$  we close the switch S. The initial current will be  $i = \frac{V_o}{R}$ , but as the capacitor charges, the voltage on the resistor will drop as well as the current.

This time the solution is:

$$V = V_o[1 - \exp(-t/\tau)]$$

Here the voltage in the capacitor will get closer and closer to the source voltage exponentially.