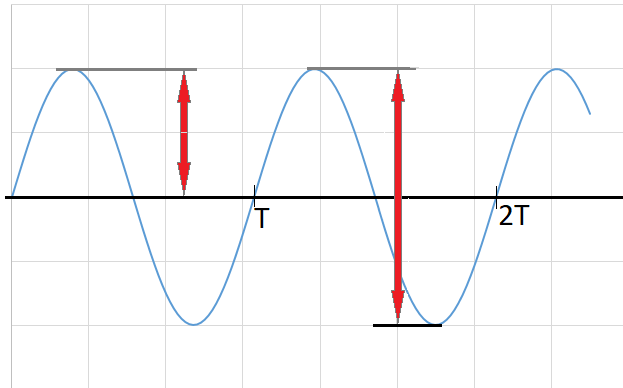


# Physics II

## Alternating currents



$$V_{\text{rms}} = \frac{V_{\text{peak}}}{\sqrt{2}}$$

rms value

$$f = \frac{1}{T}$$

frequency

$$Z = \frac{V_{\text{rms}}}{I_{\text{rms}}}$$

impedance

$$Z_C = \frac{1}{2\pi f C} \angle -90^\circ$$

impedance of a capacitor


$$Z_L = 2\pi f L \angle 90^\circ$$

impedance of an inductance

**Problem 1.-** An ac voltage, whose peak value is 125V is across a 120-Ω resistor. Find the rms voltage and the average power dissipated in the resistor.

**Problem 2.-** The specifications of an electronic instrument indicate it needs 120 V and consumes 300W of power. We understand that the voltage given is an rms quantity. If we can consider the instrument equivalent to a resistance, calculate the value of the resistance and the rms value of the current.

**Problem 3.-** The figure shows the voltage and current in an electric device. Determine the value of the impedance in magnitude and angle.

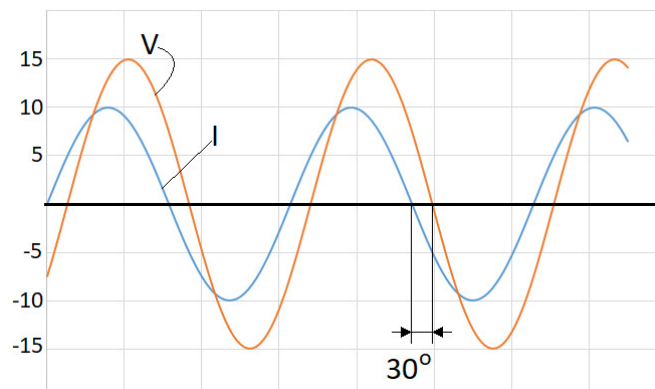

**Problem 4.-** The plate in the back of a certain computer scanner indicates the unit consumes 0.34A off a 120 V line at 60 Hz. Determine

- a) The peak current.
- b) Peak to Peak current.
- c) RMS current.
- d) The current read by an ammeter connected to the device.
- e) The amplitude of the current.
- f) The average current.
- g) The power if the phase is zero.