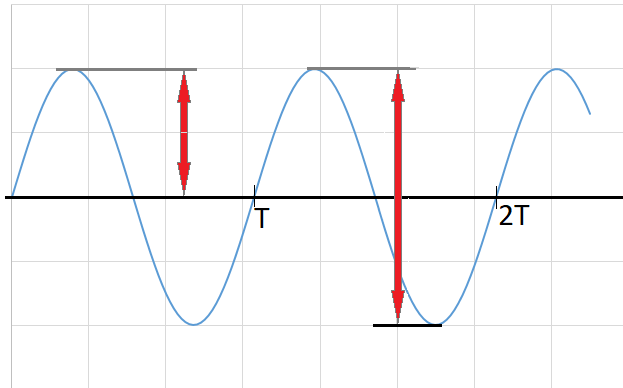


Physics II

Alternating currents



$$V_{\text{rms}} = \frac{V_{\text{peak}}}{\sqrt{2}}$$

rms value

$$f = \frac{1}{T}$$

frequency

$$Z = \frac{V_{\text{rms}}}{I_{\text{rms}}}$$

impedance

$$Z_C = \frac{1}{2\pi f C} \angle -90^\circ$$

impedance of a capacitor

$$Z_L = 2\pi f L \angle 90^\circ$$

impedance of an inductance

Problem 1.- An ac voltage, whose peak value is 125V is across a 120- Ω resistor. Find the rms voltage and the average power dissipated in the resistor.

Solution: If the peak value is 125 V, the rms value will be:

$$V_{\text{rms}} = \frac{125\text{V}}{\sqrt{2}} = \mathbf{88.4\text{ V}}$$

To calculate the power, we use the formula $\frac{V^2}{R}$ with the understanding that we should use the rms value of the voltage.

$$\text{Power} = \frac{(88.4\text{V})^2}{120\Omega} = \mathbf{65\text{ W}}$$

Problem 2.- The specifications of an electronic instrument indicate it needs 120 V and consumes 300W of power. We understand that the voltage given is an rms quantity. If we can consider the instrument equivalent to a resistance, calculate the value of the resistance and the rms value of the current.

Solution: The values given in the specifications allow us to calculate the equivalent resistance and the current:


$$P = \frac{V_{\text{rms}}^2}{R}$$

$$\rightarrow R = \frac{V_{\text{rms}}^2}{P} = \frac{(120\text{V})^2}{300\text{W}} = \mathbf{48 \Omega}$$

$$P = V_{\text{rms}} I_{\text{rms}}$$

$$\rightarrow I_{\text{rms}} = \frac{P}{V_{\text{rms}}} = \frac{300\text{W}}{120\text{V}} = \mathbf{2.5 \text{ A}}$$

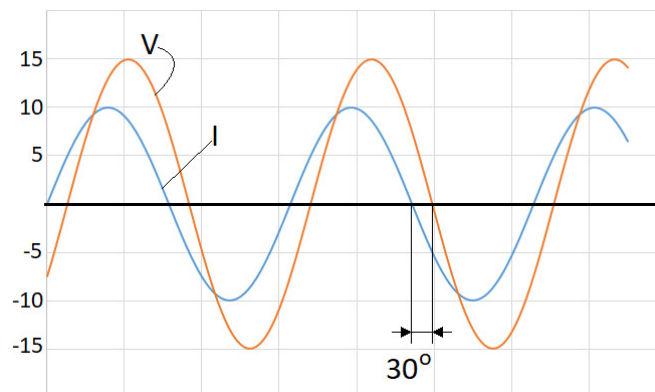Problem 3.- The figure shows the voltage and current in an electric device. Determine the value of the impedance in magnitude and angle.



Solution: By observing the values in the graph we determine:

$$Z = 1.5 \angle 30^\circ$$

Problem 4.- The plate in the back of a certain computer scanner indicates the unit consumes 0.34A off a 120 V line at 60 Hz. Determine

- The peak current.
- Peak to Peak current.
- RMS current.
- The current read by an ammeter connected to the device.
- The amplitude of the current.
- The average current.
- The power if the phase is zero.