

Physics II

Capacitor Circuits


$$C = \frac{Q}{V} \quad \text{Definition of capacitance}$$

$$C = K\epsilon_0 \frac{A}{d} \quad \text{Capacitance for parallel plates}$$


$$E = \frac{1}{2} CV^2 \quad \text{Energy stored in a capacitor}$$

Problem 1.- A $6\mu\text{F}$ capacitor is connected in series with a $12\mu\text{F}$ one. What will be the energy stored if we apply 5V to the circuit?


Problem 2.- Determine the capacitance of the following arrangement of capacitors and find how much energy is stored when you apply 10V between terminals A and B.

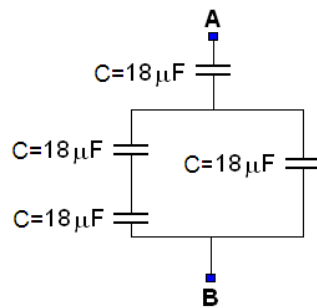

Problem 3.- Find the energy stored in the $4\mu\text{F}$ a long time after closing the switch S.

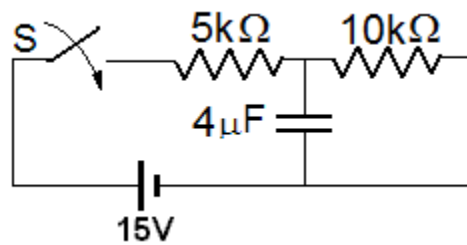

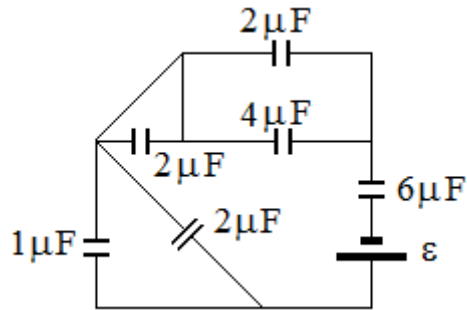Problem 4.- In the circuit shown below, the voltage in the $6\mu\text{F}$ capacitor is 4V .




Find


- The capacitance of the whole circuit.
- The source voltage.

Problem 5.- Consider the circuit shown in the figure.

- With S_1 closed and S_2 open, calculate the total capacitance.
- In that same position, calculate the total energy stored in the circuit.
- With both S_1 and S_2 closed, calculate the total capacitance.
- In this last position, calculate the total stored energy.

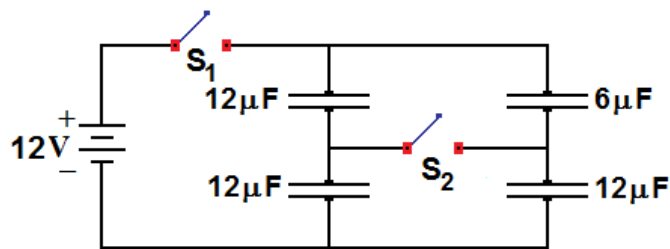

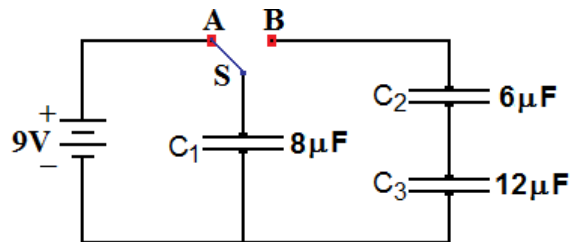
Problem 6.- In the circuit shown, S is first in A and C_2 and C_3 are initially uncharged. Then, S is switched to B , connecting C_1 with C_2 and C_3 .



Answer:

- What is the charge in C_1 when S is in A ?
- What is the charge in C_1 long after changing S to B ?
- What is the final voltage in C_1 ?
- What is the final voltage in C_2 ?
- What is the final voltage in C_3 ?

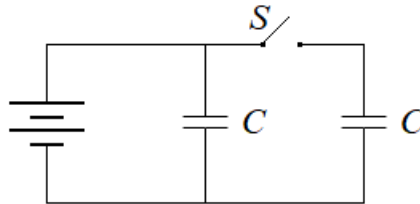Problem 7.- the figure shows two identical capacitors. Initially, with the switch S open, one capacitor is uncharged and the other has a charge Q_0 . The stored energy in this last capacitor is U_0 . The switch is closed and after a while the capacitors have charges Q_1 and Q_2 . The voltage and charge in each capacitor are V_1 , U_1 , V_2 y U_2 . Which of the following alternatives is incorrect?



(A) $Q_0 = \frac{Q_1 + Q_2}{2}$ (B) $Q_1 = Q_2$ (C) $V_1 = V_2$ (D) $U_1 = U_2$ (E) $U_0 = U_1 + U_2$

Problem 8.-

- i) Calculate the equivalent capacitance of the circuit from the terminals a and b.
- ii) Calculate the charge in each capacitor if we connect a 16V source across a and b.
- iii) Calculate the voltage across the $4\mu\text{F}$ capacitor in case (ii).

