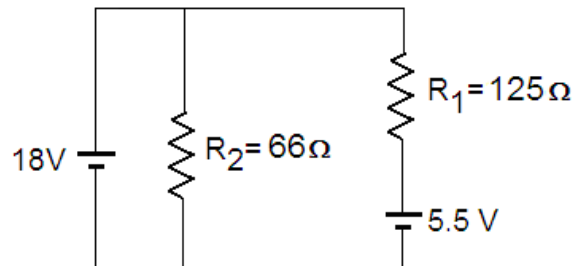



Physics II

Kirchhoff


Problem 1.- Determine the magnitude and direction (up or down) of the current through R_1 .




Problem 2.- We want to find the current through the resistors R_1 , R_2 and R_3 . Write down the equations that you need and solve the problem.

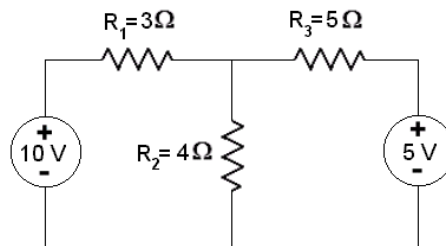


Problem 3.- Write down the equations to find the currents in the resistors. The values of the resistances are $R_1=10\Omega$, $R_2=15\Omega$ and $R_3=12\Omega$.

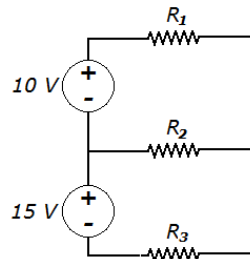


Problem 4.- Find the current through the 125Ω resistor.

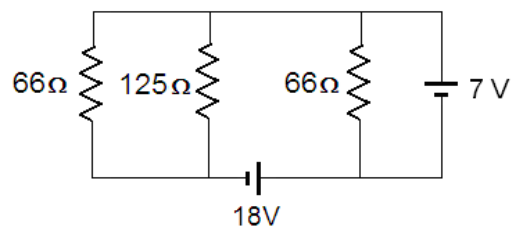


Problem 5.- Find the current through R_3 in the circuit shown:

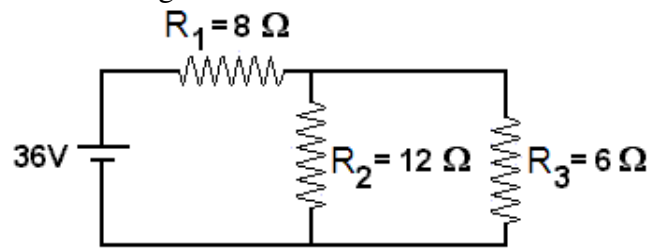

Problem 6.- Find the current through the resistors R_1 , R_2 and R_3 .

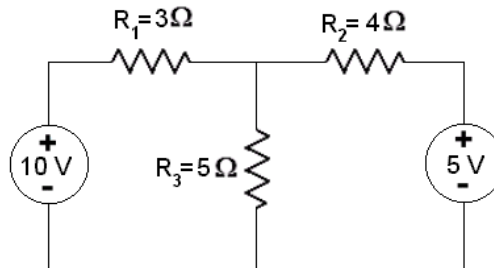

Problem 7.- Determine the magnitude and direction (left or right) of the current through R_1 .

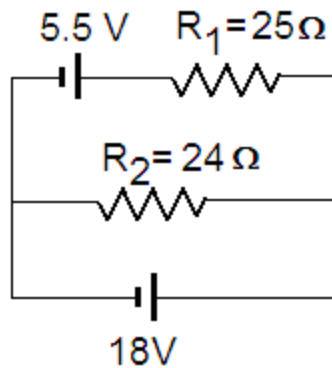

Problem 8.- In the following circuit, determine values of I_{ps} , I_1 , I_2 , V_A and V_B .

